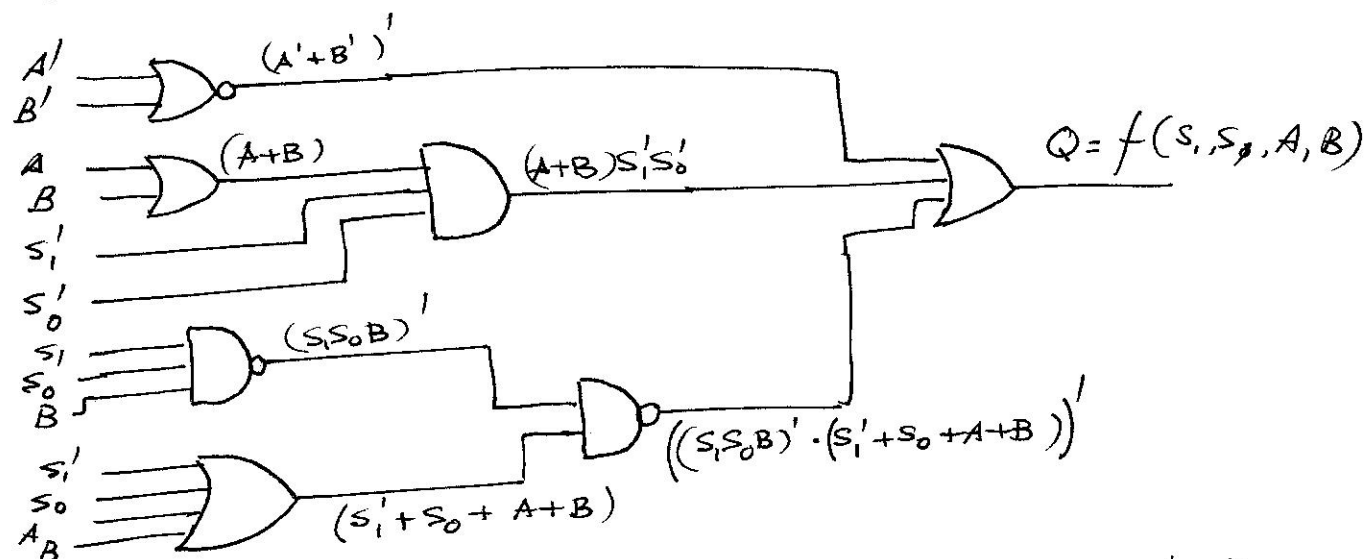


* Circuit 1B To be analysed

181



So, analysing gate by gate we produce the output Q algebraic equation, which carries the same information as the schematic

$$Q = f(S_1, S_0, A, B) = (A'+B')' + (A+B)S_1'S_0' + ((S_1S_0B)' \cdot (S_1'+S_0+A+B))'$$

So now, let's try to operate the expression to find a SoP or a PoS. Let's operate (simplify) first the big brackets:

$$(A'+B')' = A'' \cdot B'' = AB \text{ - a simple product}$$

$$(A+B)S_1'S_0' = S_1'S_0'A + S_1'S_0'B \quad (\text{Two products})$$

$$(S_1S_0B)'' + (S_1'+S_0+A+B)' = S_1S_0B + \underbrace{S_1 \cdot S_0' A' B'}_{\text{a minterm!}}$$

Finally:

$$Q = AB + S_1'S_0'B + S_1'S_0'A + S_1S_0B + S_1S_0'A'B' \quad (\text{SoP})$$

So, now let's generate the sum of minterms, which happens to be all the terms '1' in the truth table. Let's add the missing variables term by term:

$$AB = AB(S_1+S_1') = ABS_1 + ABS_1'$$

$$\begin{array}{ccc} \swarrow \downarrow & & \downarrow \\ S_1S_0AB & + & S_1S_0'AB & & S_1'S_0AB & + & S_1'S_0'AB \end{array}$$

$$m_{911} + m_{1011} + m_{0111} + m_{0011}$$

$$m_{15} + m_{11} + m_7 + m_3$$

$$S_1' S_0' B = S_1' S_0' A B + S_1' S_0' A' B = m_{0011} + m_{0001}$$

$m_3 \quad m_1$

$$S_1' S_0' A \Rightarrow S_1' S_0' A B + S_1' S_0' A B' \rightarrow m_{0011} + m_{0010}$$

$m_3 \quad m_2$

$$S_1 S_0 B = S_1 S_0 A B + S_1 S_0 A' B = m_{1111} + m_{1101}$$

$m_{15} + m_{13}$

$\hookrightarrow S_1 S_0 (A + A') B$

$$S_1 S_0' A' B' = m_{1000} \rightarrow m_8$$

In this way:

$$Q = f(S_1, S_0, A, B) = \sum_4 m(1, 2, 3, 7, 8, 11, 13, 15)$$

and also:

$$= \prod_4 M(0, 4, 5, 6, 9, 10, 12, 14)$$

and the truth table is the same information, or the Karnaugh map:

S_1	S_0	A	B	Q
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

$S_1 \backslash S_0 \backslash A \backslash B$	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	1	1	0
10	1	0	1	0

we are not going to use it.
Instead, we'll minimize
functions using software like
minilog.exe